

# Lecture 2:



# Sequential Networks and Finite State Machines

John Eldon  
University of California, San Diego

# Outline

- Specification: Finite State Machine
  - State Table, State Diagram, Behavior
- Implementation
  - Excitation Table
  - Mealy and Moore Machines
  - Examples

# Sequential Networks

  

RTL: Register-Transfer Level Description

1. Gray: DFFs = "registers"
2. Specification: What does it do?
3. Implementation: Excitation or Transition Table

# Specification

- Combinational Logic
  - Truth Table
  - Boolean Expression
  - Logic Diagram (No feedback loops)
- Sequential Networks:
  - State Diagram, State Assignment, State Table
  - Excitation Table and Characteristic Expression
  - Logic Diagram (FFs and feedback loops)

# Implementation: Design Flow

- Input-Output Relation
- State Diagram (Transition of states)
- State Assignment (Map states into binary code)
- State Table (Truth table of states)
- Excitation Table (Truth table of FF inputs)
- Boolean Expression
- Logic Diagram

# Implementation: Design Flow

- Input Output Relation
- State Diagram (Transition of states)
  - State minimization (Reduction)
  - Finite state machine partitioning
- State Assignment (Map states into binary code)
  - Binary code, Gray encoding, One hot encoding, Coding optimization
- State Table (Truth table of states)
- Excitation Table (Truth table of FF inputs)

# Implementation: Examples


- Example 1: a circuit with D Flip Flops
- Example 2: a circuit with other Flip Flops
- Example 3: analysis of a sequential machine

# State: What is it? Why do we need it?

Symbol/ Circuit



Behavior over time

 

What is the expected output of the counter over time?




# Finite State Machines: Describing circuit behavior over time

 Symbol/ Circuit

 


Diagram that depicts behavior over time



# Implementing the 2 bit counter

State Diagram



State Table: Symbol

Current state	Next State
$S_0$	$S_1$
$S_1$	$S_2$
$S_2$	$S_3$
$S_3$	$S_0$


State  
Assignment

State	$Q_1$	$Q_0$
$S_0$	0	0
$S_1$	0	1
$S_2$	1	0
$S_3$	1	1

$Q_1(t)$	$Q_0(t)$	$Q_1(t+1)$	$Q_0(t+1)$

State Table: Binary

# Implementing the 2 bit counter

 

State Diagram

Current state	Next State
$S_0$	$S_1$
$S_1$	$S_2$
$S_2$	$S_3$
$S_3$	$S_0$

$Q_1(t)$	$Q_0(t)$	$Q_1(t+1)$	$Q_0(t+1)$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0


State Table

# State Table

$Q_1(t)$	$Q_0(t)$	$Q_1(t+1)$	$Q_0(t+1)$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

$$D_0(t) = Q_0(t)'$$
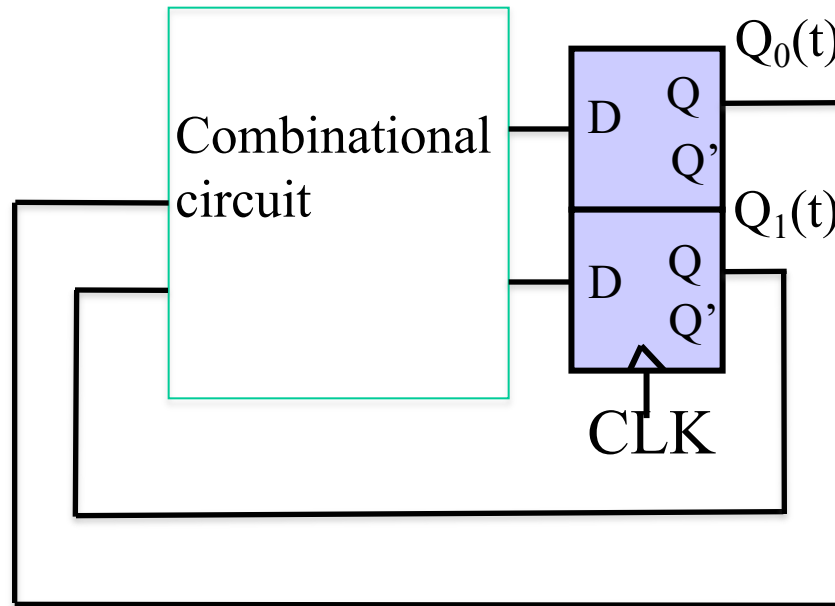
$$D_1(t) = Q_0(t) Q_1(t)' + Q_0(t)' Q_1(t)$$



Circuit with 2 flip flops


$Q_1(t)$	$Q_0(t)$	$Q_1(t+1)$	$Q_0(t+1)$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

State Table

Truth table→K map→Switching function

$$Q_0(t+1) = Q_0(t)'$$
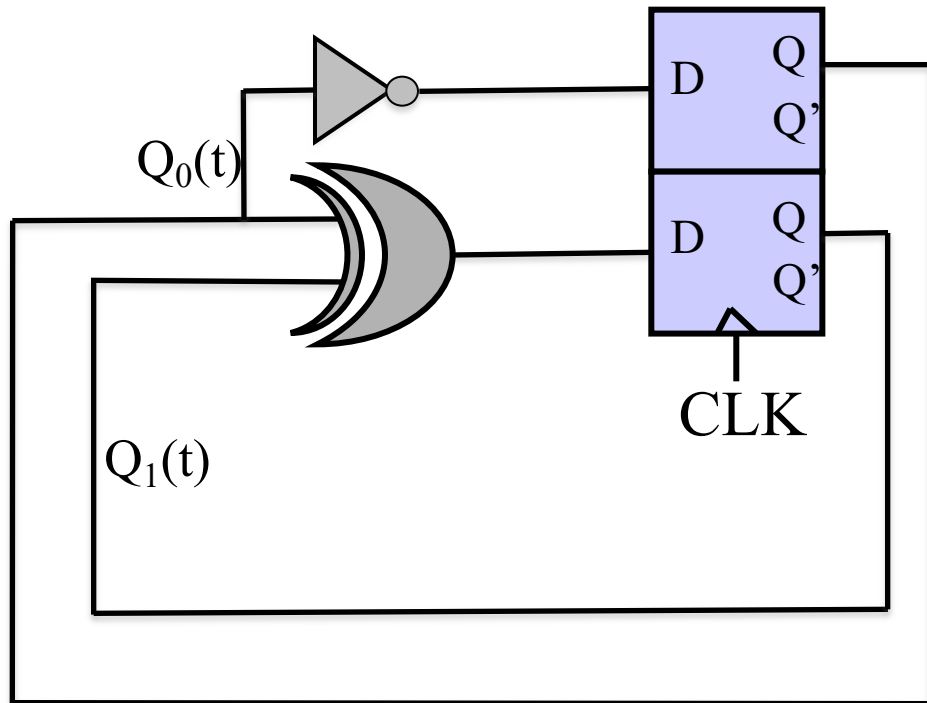
$$Q_1(t+1) = Q_0(t) Q_1(t)' + Q_0(t)' Q_1(t)$$




Implementation of 2-bit counter

We store the current state using D-flip flops so that:


- Inputs to this combinational circuit don't change while the next output is being computed (free-running).
- The transition to the next state occurs only at rising edge of clock.
- Skip the K map & logic optimization and let the synthesizer do it.
- Revisit by hand if not meeting timing.
 
# Generalized Model of Sequential Circuits



Netlist  $\Leftrightarrow$  State Table  $\Leftrightarrow$  State Diagram  $\Leftrightarrow$  Input Output Relation

PS\Input	X=0	X=1
S0	S0,0	S2,0
S1	S3,0	S3,0
S2	S2,0	S1,0
S3	S1,1	S0,1

 


Example: Output sequence

Time	0	1	2	3	4	5
Input	0	1	1	0	1	-
State	S0					
Output						

Netlist  $\Leftrightarrow$  State Table  $\Leftrightarrow$  State Diagram  $\Leftrightarrow$  Input Output Relation

PS\Input	X=0	X=1
S0	S0,0	S2,0
S1	S3,0	S3,0
S2	S2,0	S1,0
S3	S1,1	S0,1

 

Example: Output sequence

Time	0	1	2	3	4	5
Input	0	1	1	0	1	-
State	S0	S0	S2	S1	S3	S0
Output	0	0	0	0	1	0




# Implementation

State Diagram  $\Rightarrow$  State Table  $\Rightarrow$  Logic Diagram

- Canonical Form: Mealy and Moore Machines
  - Mealy machines: General
  - Moore machines: Output is independent of current input (subset of Mealy).
- Excitation Table
  - Truth Table of the F-F Inputs
  - Boolean algebra, K-maps for combinational logic
- Examples
- Timing


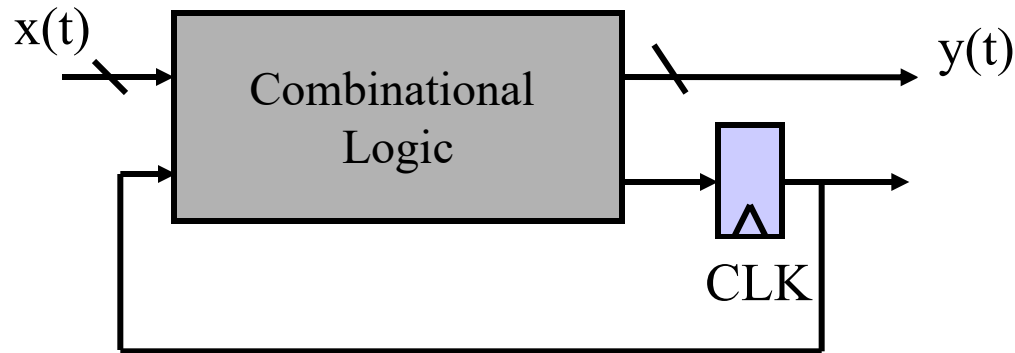
# Canonical Form: Mealy and Moore Machines



e.g., Traffic Light Controller:

C1 = brains

C2 maps state to lights themselves

  


# Canonical Form: Mealy and Moore Machines


Mealy Machine:  $y_i(t) = f_i(X(t), S(t))$

Moore Machine:  $y_i(t) = f_i(S(t))$

$$s_i(t+1) = g_i(X(t), S(t))$$

 

Mealy Machine

 

Moore Machine


often  $C2 = \text{wire} \rightarrow$   
output is synchronous w/  $CLK$

# Canonical Form: Mealy and Moore Machines


Mealy Machine:  $y_i(t) = f_i(X(t), S(t))$

Moore Machine:  $y_i(t) = f_i(S(t))$

$s_i(t+1) = g_i(X(t), S(t))$

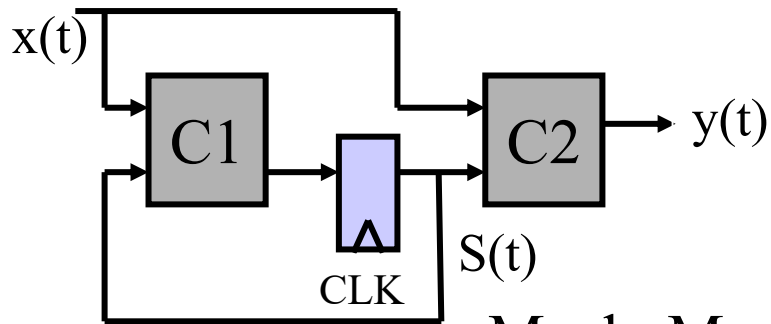



Mealy Machine

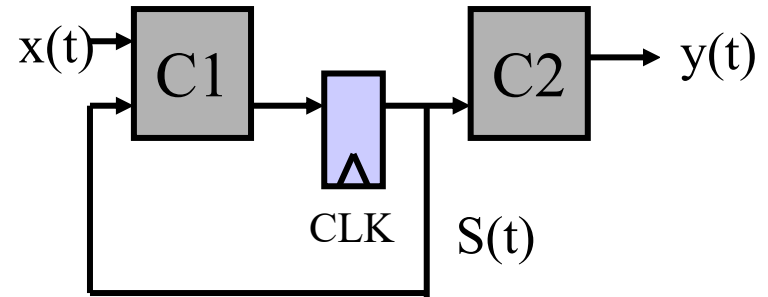

Moore Machine

	Input
PS	NS, output

	Input	
PS	NS	Output

  

# Life on Mars?

Mars rover has a binary input  $x$ . When it receives the input sequence  $x(t-2, t) = 001^*$  from its life detection sensors, it means that it has detected life on Mars ☺ and the output  $y(t) = 1$ ; otherwise  $y(t) = 0$  (no life on Mars ☹).

---

\* Think of Binary Phase Shift Keying. To send a 0, don't invert the sinusoidal carrier. To send a 1, invert the sinusoidal carrier (phase shift 180 degrees) for the duration of the 1. Narrow-band: symbol (data bit) duration  $\gg$  carrier cycle time. Ultrawideband (UWB) -- modulation frequency might be only about 1/3 of carrier frequency.

Implement the Life-on-Mars  
Pattern Recognizer!



# *The* WAR of the WORLDS

*By H. G. Wells*


Author of "Under the Knife," "The Time Machine," etc.




# Mars Life Recognizer FSM

Which of the following diagrams is a correct Mealy solution for the 001 pattern recognizer on the Mars rover?

A.

 

B.

 


C. Both A and B are correct


D. None of the above

# Mars Life Recognizer FFs

Pattern Recognizer '001'

 

Mealy Machine


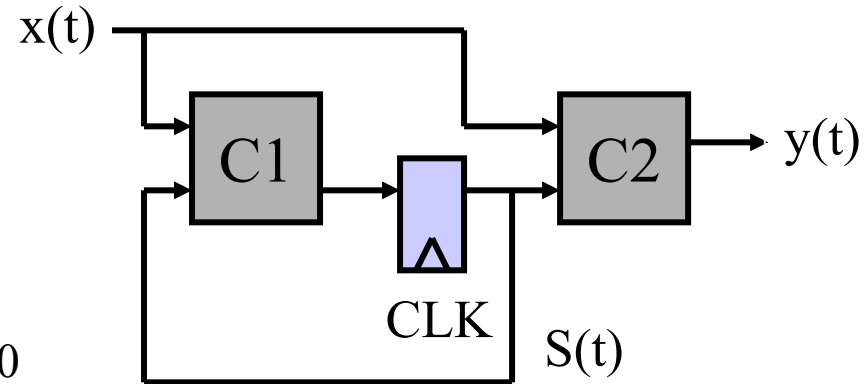


What does state table need to show to design controls of C1?

- A. next state  $S(t+1)$  vs. input  $x(t)$ , and present state  $S(t)$
- B. output  $y(t)$  vs. input  $x(t)$ , and present state  $S(t)$
- C. output  $y(t)$  vs. present state  $S(t)$
- D. None of the above


  
# State Diagram $\Rightarrow$ State Table with State Assignment



$S(t) \backslash x$	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S0,1

State Assignment

S0: 00

S1: 01


S2: 10

$S(t) \backslash x$	0	1
00	01,0	00,0
01	10,0	00,0
10	10,0	00,1

$Q_1(t+1)Q_0(t+1), y$

# State Diagram => State Table => Excitation Table => Circuit

$Q_1(t) Q_0(t) \backslash x$	0	1
00	01,0	00,0
01	10,0	00,0
10	10,0	00,1

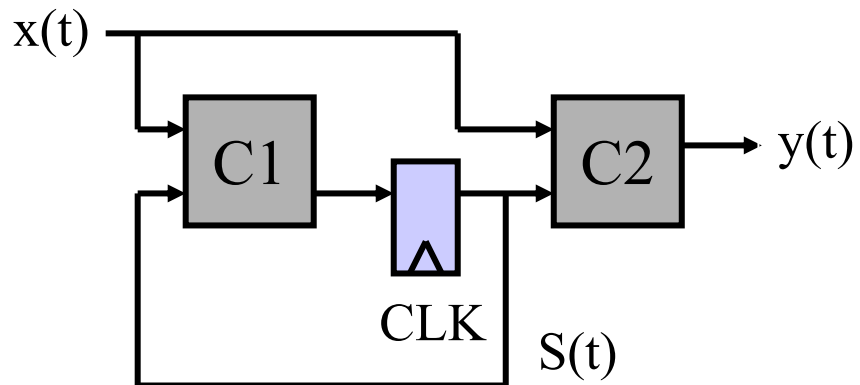


Mealy Machine

id	$Q_1 Q_0 x$	$D_1$	$D_0$	$y$
0	000	0	1	0
1	001	0	0	0
2	010	1	0	0
3	011	0	0	0
4	100	1	0	0
5	101	0	0	1
6	110			
7	111			

State Diagram => State Table => Excitation Table => Circuit

$Q_1(t) Q_0(t) \backslash x$	0	1
00	01,0	00,0
01	10,0	00,0
10	10,0	00,1

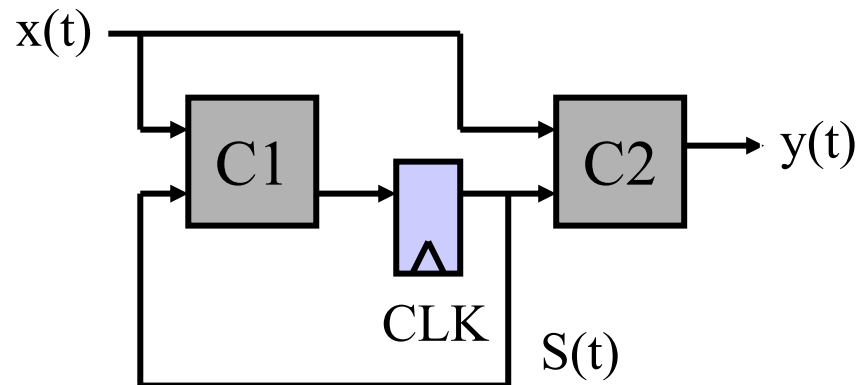

Mealy Machine

id	$Q_1 Q_0 x$	$D_1$	$D_0$	y
0	000	0	1	0
1	001	0	0	0
2	010	1	0	0
3	011	0	0	0
4	100	1	0	0
5	101	0	0	1
6	110			
7	111			

Fill in rows 6 and 7 of excitation table

A. All 0s

B. All 1s

C. All Don't Cares

State Diagram => State Table => Excitation Table => **Circuit**

id	$Q_1Q_0x$	$D_1$	$D_0$	$y$
0	000	0	1	0
1	001	0	0	0
2	010	1	0	0
3	011	0	0	0
4	100	1	0	0
5	101	0	0	1
6	110	X	X	X
7	111	X	X	X

$D_1(t)$ :


		$Q_0$	
$x(t)$	<sup>0</sup> 0	<sup>2</sup> 1	<sup>6</sup> X
	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup> X
		$Q_1$	
		<sup>4</sup> 1	<sup>5</sup> 0

$$D_1(t) = x'Q_0 + x'Q_1$$

$$D_0(t) = Q_1'Q_0'x'$$

$$y = Q_1x$$

 
State Diagram => State Table => Excitation Table => **Circuit**



$$D_1(t) = x'Q_0 + x'Q_1$$

$$D_0(t) = Q'_1Q'_0x'$$


$$y = Q_1x$$

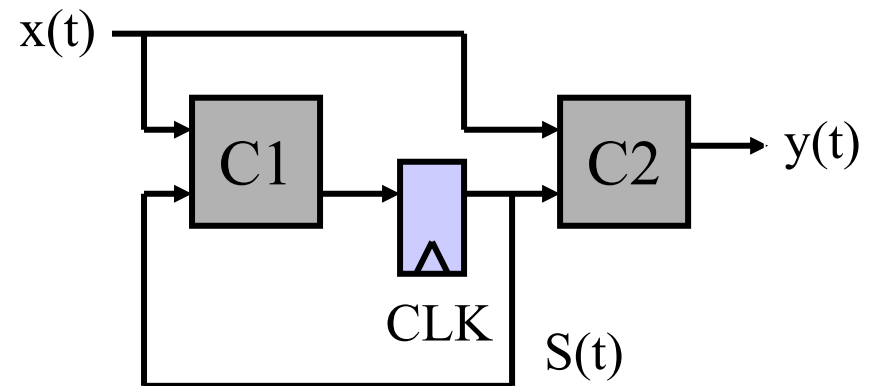

Mealy Machine
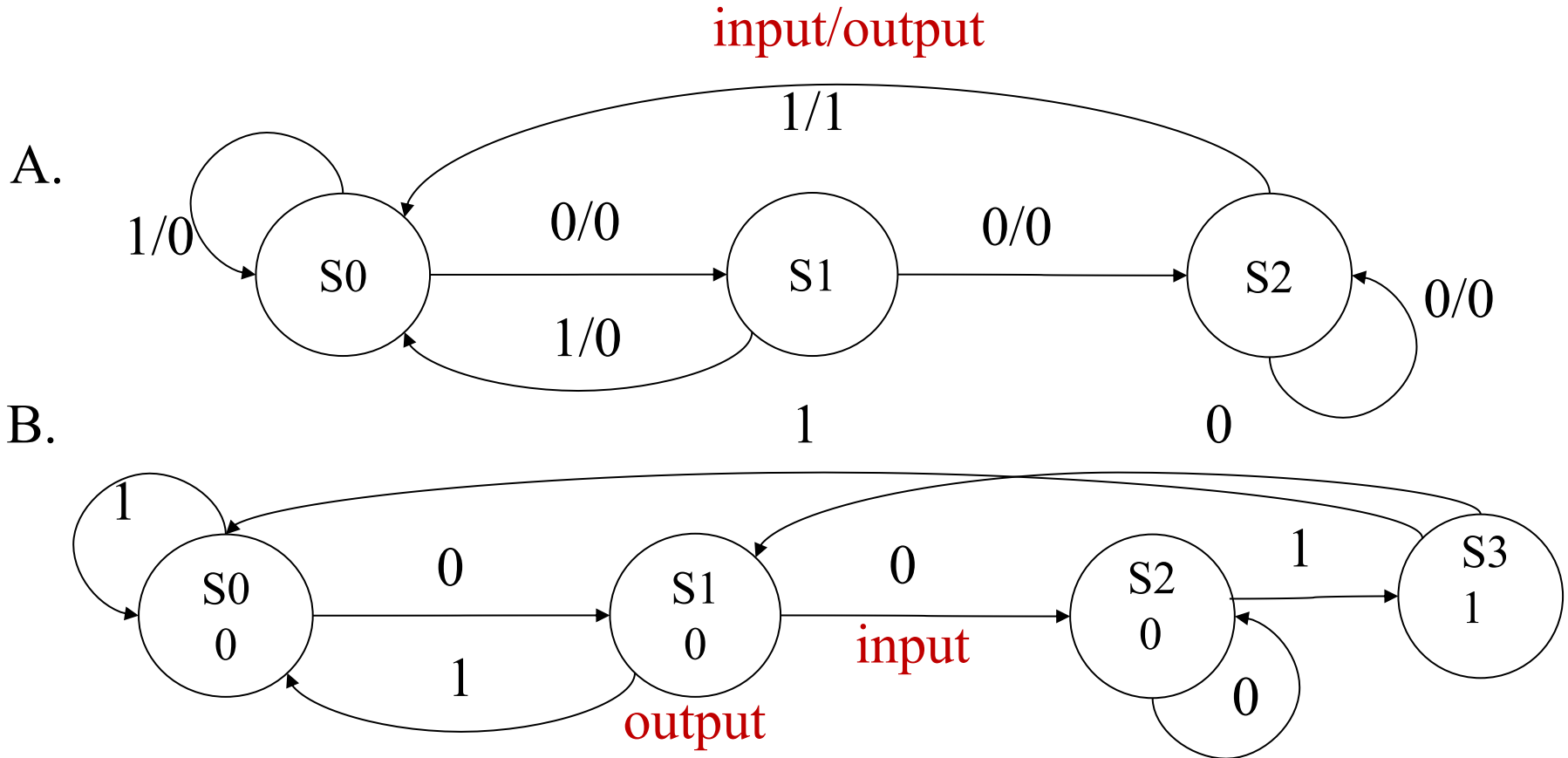
# Moore FSM for the Mars Life Recognizer


Which of the following diagrams is a correct Moore solution to the '001' pattern recognizer?



- C. Both A and B are correct
- D. None of the above

# Moore Mars Life Recognizer: FF Input Specs


Pattern Recognizer '001'

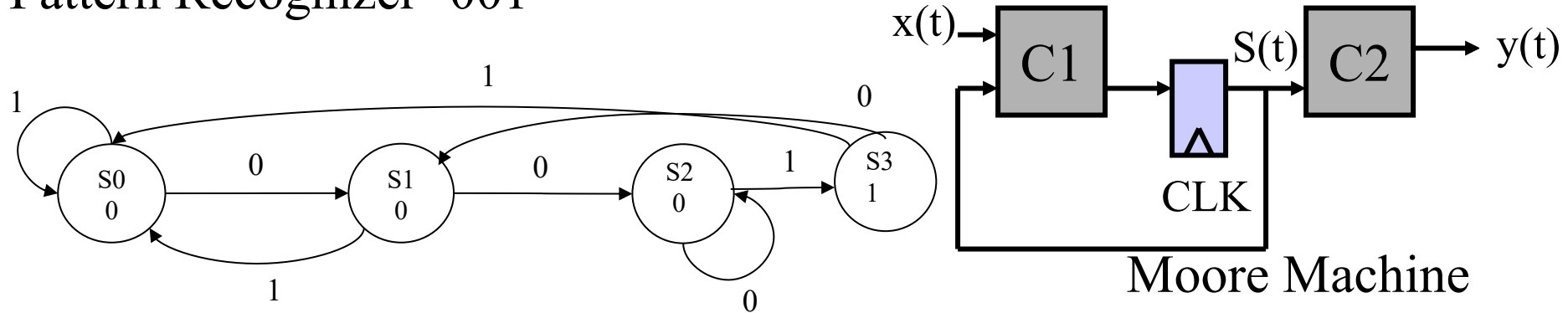

What does state table need to show to design controls of  $C2$ ?

- A. (current input  $x(t)$ , current state  $S(t)$  vs. next state,  $S(t+1)$ )
- B. (current input, current state vs. current output  $y(t)$ )
- C. (current state vs. current output  $y(t)$  and next state)
- D. (current state vs. current output  $y(t)$  )
- E. None of the above
 
# Moore Mars Life Recognizer: State Table



S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S3,0
S3	S1,1	S0,1

Q <sub>1</sub> Q <sub>0</sub> \x	0	1
00	01,0	00,0
01	10,0	00,0
10	10,0	11,0
11	01,1	00,1

ID	Q <sub>1</sub> Q <sub>0</sub> x	D <sub>1</sub>	D <sub>0</sub>	y
0	000	0	1	0
1	001	0	0	0
2	010	1	0	0
3	011	0	0	0
4	100	1	0	0
5	101	1	1	0
6	110	0	1	1
7	111	0	0	1

Q<sub>1</sub>(t+1)Q<sub>0</sub>(t+1), y



# Mars Life Recognizer: Circuit Design

id	$Q_1Q_0x$	$D_1$	$D_0$	$y$
0	000	0	1	0
1	001	0	0	0
2	010	1	0	0
3	011	0	0	0
4	100	1	0	0
5	101	1	1	0
6	110	0	1	1
7	111	0	0	1

$D_1(t)$ :

	$Q_0$			
$x(t)$	<sup>0</sup> 0	<sup>2</sup> 1	<sup>6</sup> 0	<sup>4</sup> 1
	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup> 0	<sup>5</sup> 1
	$Q_1$			

$D_0(t)$ :


	$Q_0$			
$x(t)$	<sup>0</sup> 1	<sup>2</sup> 0	<sup>6</sup> 1	<sup>4</sup> 0
	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup> 0	<sup>5</sup> 1
	$Q_1$			

$y(t)$ :

	$Q_0$			
$x(t)$	<sup>0</sup> 0	<sup>2</sup> 0	<sup>6</sup> 1	<sup>4</sup> 0
	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup> 1	<sup>5</sup> 0
	$Q_1$			
 
# Mars Life Recognizer Circuit Implementation


State Diagram => State Table => Excitation Table => **Circuit**



$$D_1(t) = Q_1(t)Q_0(t)' + Q_1(t)'Q_0(t)x(t)$$


$$D_0(t) = Q_1(t)'Q_0(t)'x(t)' + Q_1(t)Q_0(t)x(t)' + Q_1(t)Q_0(t)'x(t)$$

$$y(t) = Q_1(t)Q_0(t)$$

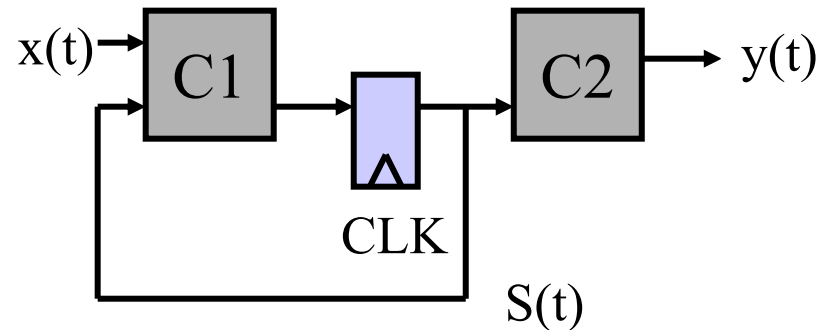


Moore Machine

# Conversion from Mealy to Moore Machine

 

$S(t) \backslash x$	0	1
$S_0$	$S_1, 0$	$S_0, 0$
$S_1$	$S_2, 0$	$S_0, 0$
$S_2$	$S_2, 0$	$S_0, 1$

 

$S(t) \backslash x$	0	1
$S_0$	$S_1, 0$	$S_0, 0$
$S_1$	$S_2, 0$	$S_0, 0$
$S_2$	$S_2, 0$	$S_3, 0$
$S_3$	$S_1, 1$	$S_0, 1$

# Conversion from Mealy to Moore Machine

S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	<b>S0,1</b>

S(t)\x	0	1	y
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
<b>S3</b>			

## Algorithm

1. Identify distinct (NS, y) pair
2. Replace each distinct (NS, y) pair with distinct new states
3. Insert rows of present state = new states

# Conversion from Mealy to Moore Machine

Mealy	S(t)\x	0	1
	S0	S1,0	S0,0
	S1	S2,0	S0,0
	S2	S2,0	<b>S0,1</b>

	S(t)\x	0	1	y
	S0	S1	S0	0
	S1	S2	S0	0
	S2	S2	<b>S3</b>	0
	<b>S3</b>			


 Moore |

1. Find distinct NS, y
2. Add new states to represent distinct NS, y


For the above Moore machine, what are the next states with respect to present state S3?

- A.S2, S3, 1
- B.S2, S0, 1
- C.S1, S0, 1
- D.S1, S0. 0
- E.None of the above.

# Conversion from Mealy to Moore Machine

 


S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S0,1

 


S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S3,0
S3	S1,1	S0,1

Time	0	1	2	3	4	5	6	7	8
x	0	1	0	0	1	1	0	0	1
S <sub>mealy</sub>	S0	S1	S0	S1	S2	S0	S0	S1	S2
y <sub>mealy</sub>									
S <sub>moore</sub>	S0								
y <sub>moore</sub>									

# Conversion from Mealy to Moore Machine

 

S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S0,1

 


S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S3,0
S3	S1,1	S0,1

Time	0	1	2	3	4	5	6	7	8
x	0	1	0	0	1	1	0	0	1
S <sub>mealy</sub>	S0	S1	S0	S1	S2	S0	S0	S1	S2
y <sub>mealy</sub>									
S <sub>moore</sub>	S0								
y <sub>moore</sub>									


iClicker S<sub>moore</sub>[0-5]

- A. S0,S1,S0,S1,S2,S3
- B. S0,S1,S0,S1,S2,S0
- C. S3,S1,S0,S1,S2,S3
- D. S3,S1,S0,S1,S2,S0
- E. None of the above

# Conversion from Mealy to Moore Machine

 

S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S0,1

 

S(t)\x	0	1
S0	S1,0	S0,0
S1	S2,0	S0,0
S2	S2,0	S3,0
S3	S1,1	S0,1

Time	0	1	2	3	4	5	6	7	8
x	0	1	0	0	1	1	0	0	1
S <sub>mealy</sub>	S0	S1	S0	S1	S2	S0	S0	S1	S2
y <sub>mealy</sub>									
S <sub>moore</sub>	S0								
y <sub>moore</sub>									

$y_{\text{moore}}[0-5]$

A. 0,0,0,0,1,0

B. 0,0,0,0,0,1

C. 0,1,0,0,0,0

D. 0,0,0,0,0,0,

E. None of the above




# Conversion from Mealy to Moore Machine

## Algorithm

1. Identify distinct (NS, y) pair
2. Replace each distinct (NS, y) pair with distinct **new states**
3. Insert rows of present state = **new states**
4. Append each present state with its output y

 
# Finite State Machine Example

- Traffic light controller
  - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - Lights:  $L_A$ ,  $L_B$



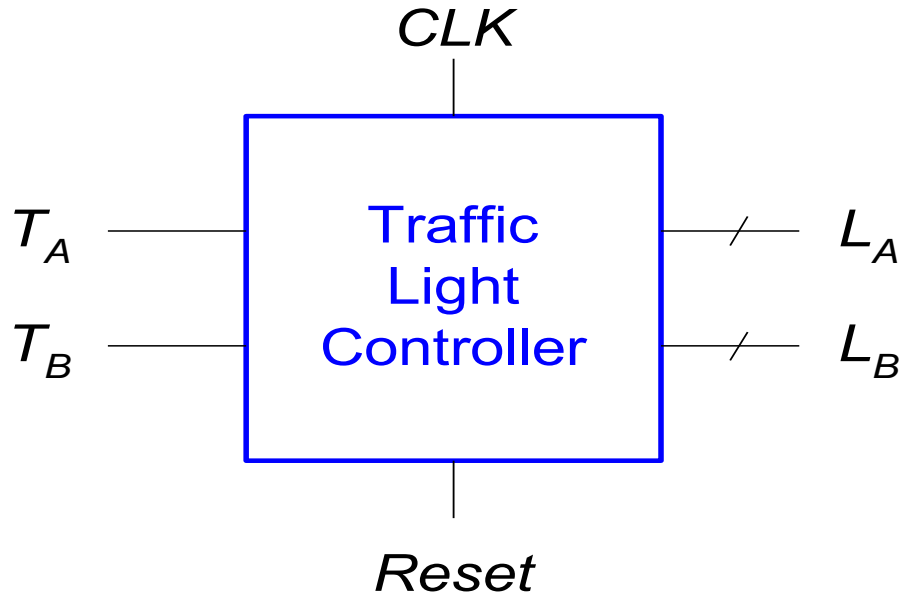
# FSM Black Box

- Inputs:  $CLK$ ,  $Reset$ ,  $T_A$ ,  $T_B$
- Outputs:  $L_A$ ,  $L_B$



 
# FSM State Transition Diagram

- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs


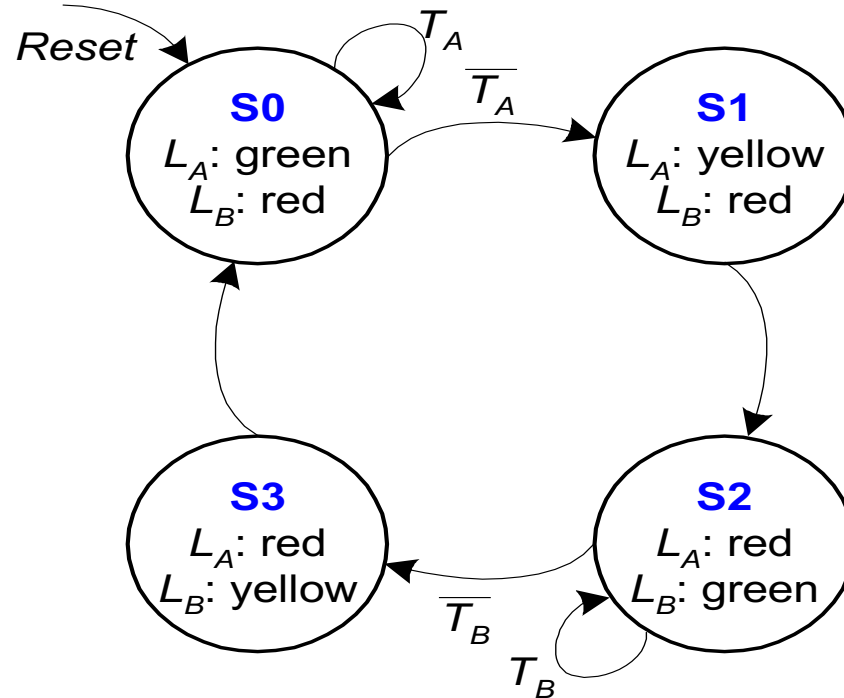
# FSM State Transition Diagram

- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



# FSM State Transition Table

PS	Inputs		NS
	$T_A$	$T_B$	
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

# State Transition Table

PS		Inputs		NS	
$Q_1(t)$	$Q_0(t)$	$T_A$	$T_B$	$Q_1(t+1)$	$Q_0(t+1)$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$Q_1(t+1) = Q_1(t) \oplus Q_0(t)$$

$$Q_0(t+1) = Q_1'(t)Q_0'(t)T_A' + Q_1(t)Q_0'(t)T_B'$$

# FSM Output Table

PS		Outputs			
$Q_1$	$Q_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = Q_1$$


$$L_{A0} = Q_1' Q_0$$

$$L_{B1} = Q_1'$$


$$L_{B0} = Q_1 Q_0$$




# FSM Schematic: State Register

 

# Logic Diagram

 

# FSM Schematic: Output Logic

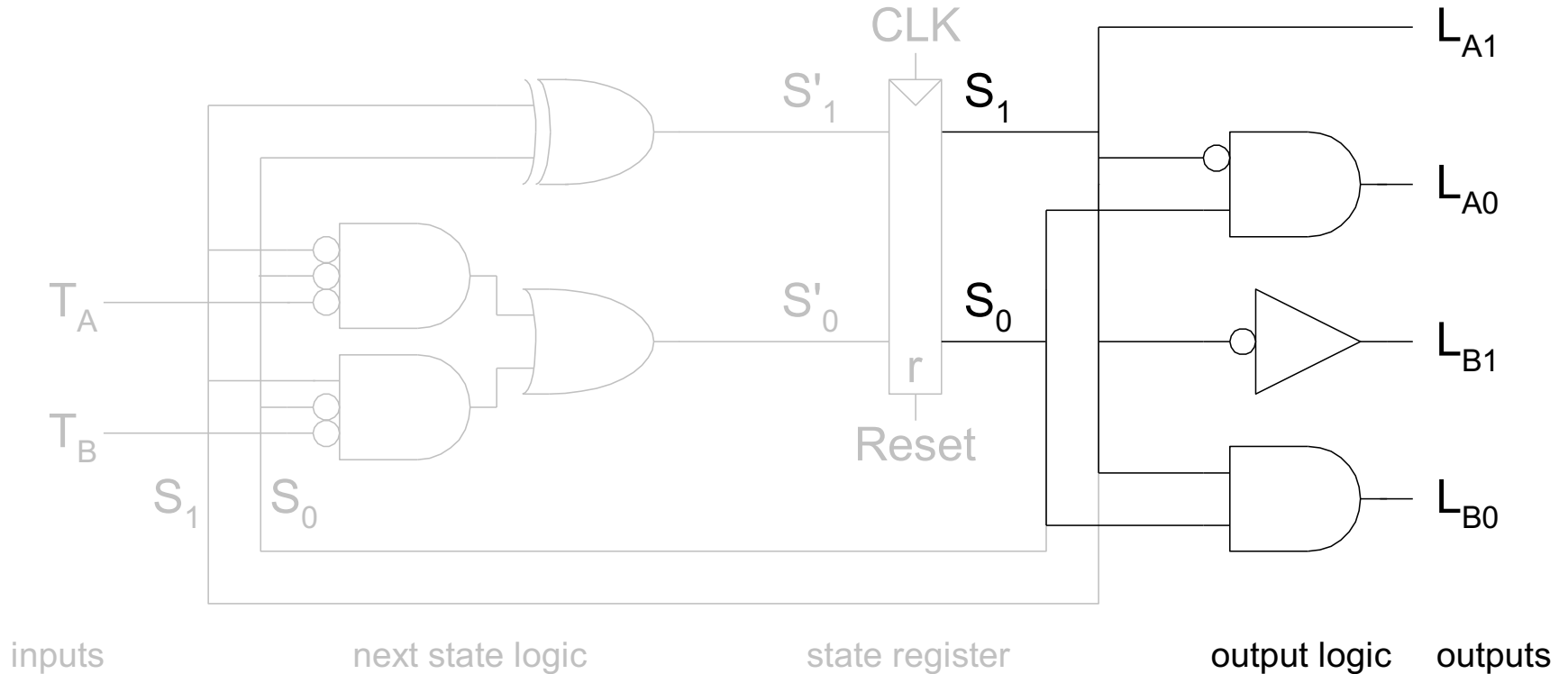

# Summary: Implementation

- Set up canonical form
  - Mealy or Moore machine
- Identify the next states
  - state diagram  $\Rightarrow$  state table
  - state assignment
- Derive excitation table
  - Inputs of flip flops
- Design the combinational logic
  - don't care set utilization